

EE214 - Report 4

Implementing BCD Adder

Harsh S Roniyar (22B3942)
FR-19/T-19

01st September 2023

Contents

1	K-Maps and Circuit Diagrams	3
2	BCD Adder	5

Introduction

In this report, I have presented my work done on Quartus using VHDL during the third lab.

I have also done design verification using ScanChain tool on Xen-10 FPGA board and verified my design.

The circuit presented in the report has the RTL Viewer followed by the ModelSim Waveform obtained from Quartus.

Chapter 1

K-Maps and Circuit Diagrams

This section contains the k-map and the diagram of the circuit made in the lab.

01/09/2023

Week 4: Problem - Set 4

M	T	W	T	F	S	S
Page No.						YOUVA
Date:						

→ BCD Adder

$Y(4) = S_1(2) S_1(3) + S_1(3) S_1(1) + C_1$

K-map

$S_1 \backslash S_2$	00	01	11	10
00	0	0	0	0
01	0	0	1	1
11	1	1	1	1
10	1	1	1	1

~~XXXX~~

tanishk
 1 sep 2023

Chapter 2

BCD Adder

The concept of BCDAdder was to take in 2 4-bit decimal numbers (0 to 9) and then adding them such that the output also followed the BCD system.

A few examples to demonstrate BCD Addition.


A(3)	A(2)	A(1)	A(0)	B(3)	B(2)	B(1)	B(0)	Y(4)	Y(3)	Y(2)	Y(1)	Y(0)	Decimal
0	0	1	0	0	0	1	1	0	0	1	0	1	09
1	0	0	1	0	1	0	0	1	0	0	1	1	13
1	0	0	0	0	1	1	1	1	0	1	0	1	15
1	0	0	1	1	0	0	1	1	1	0	0	0	18


Table 2.1: Some of the input-output mappings of a BCDAdder

I used the 4-bit Full Adder-Subtractor (also called as Ripple Adder) and the basic gates to implement the BCD Adder Circuit which can be seen in the RTL Viewer in the following page.

Date: September 02, 2023

Project: BCDAdder

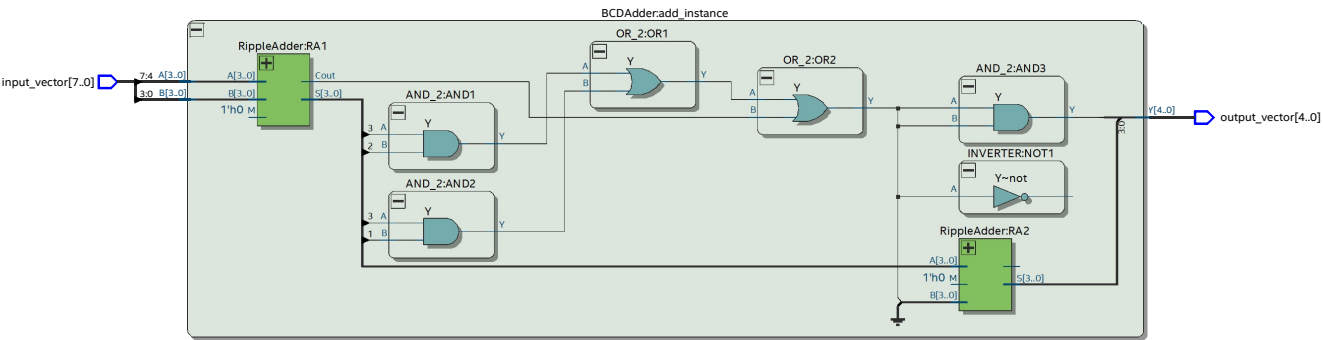

 

THANK YOU!